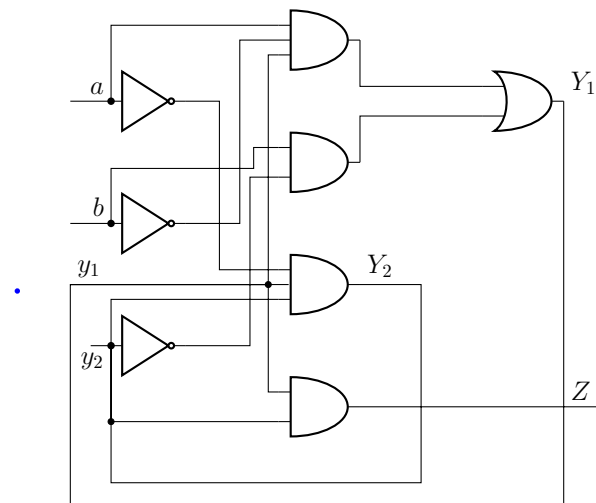


TP 4  
Digital Electronics [ELEC-H-310]  
Correction  
v1.0.1

**Question 1.** What are the logic equations for this circuit? Fill a Huffman table and find the corresponding state graph.

a)



**Answer:**

$$Y_1 = a\bar{b}y_1 + b\bar{y}_2$$

$$Y_2 = \bar{a}y_1y_2$$

$$Z = y_1y_2$$


	$ab$				
$Y_1Y_2$	00	01	11	10	$Z$
00	00	10	10	00	0
01	00	00	00	00	0
11	01	01	00	10	1
10	00	10	10	10	0


$$1. a) y_1 = (a \cdot \overline{b} y_1) + b \overline{y_2}$$

$$y_2 = \overline{a} y_1 y_2$$


$$z = y_1 y_2$$

	a b				z
$y_1 y_2$	00	01	11	10	
00	00	10	10	00	0
01	00	00	00	00	0
11	01	01	00	10	1
10	00	10	10	10	0

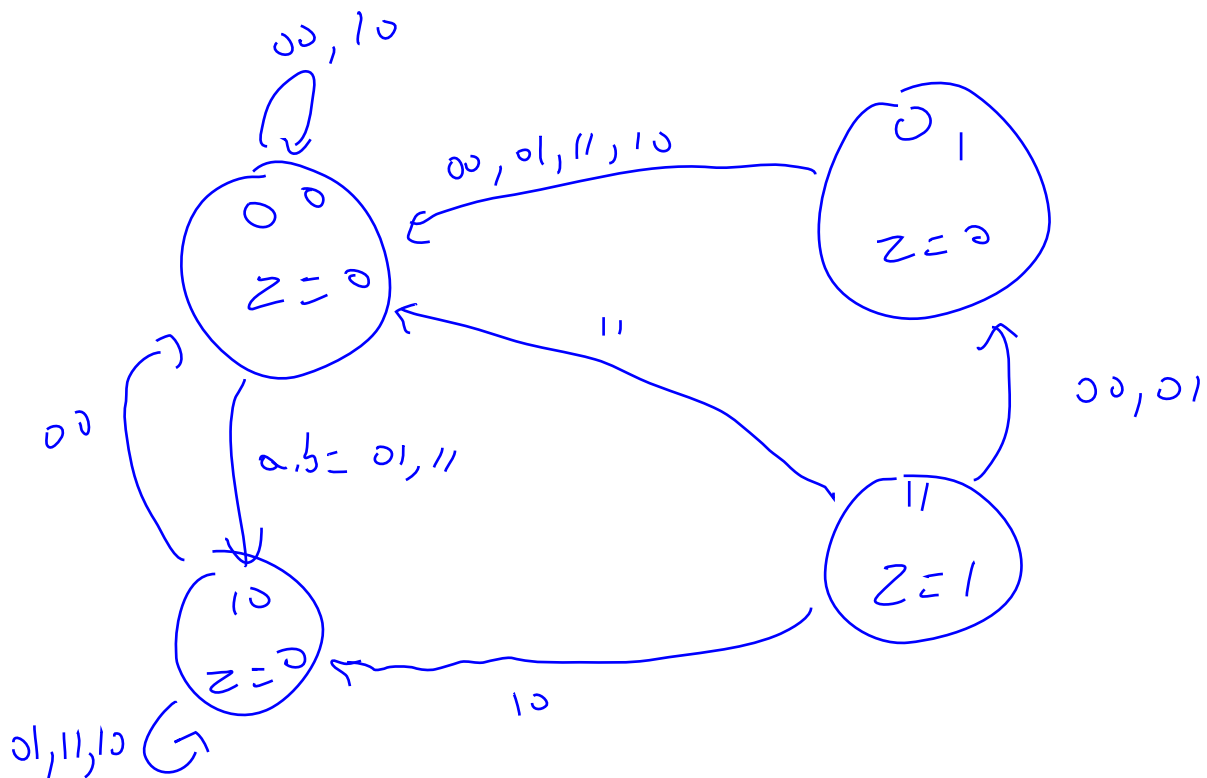

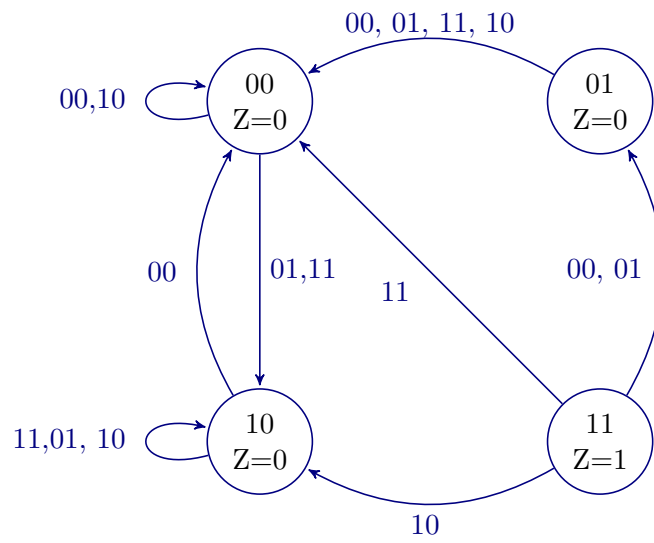

b)

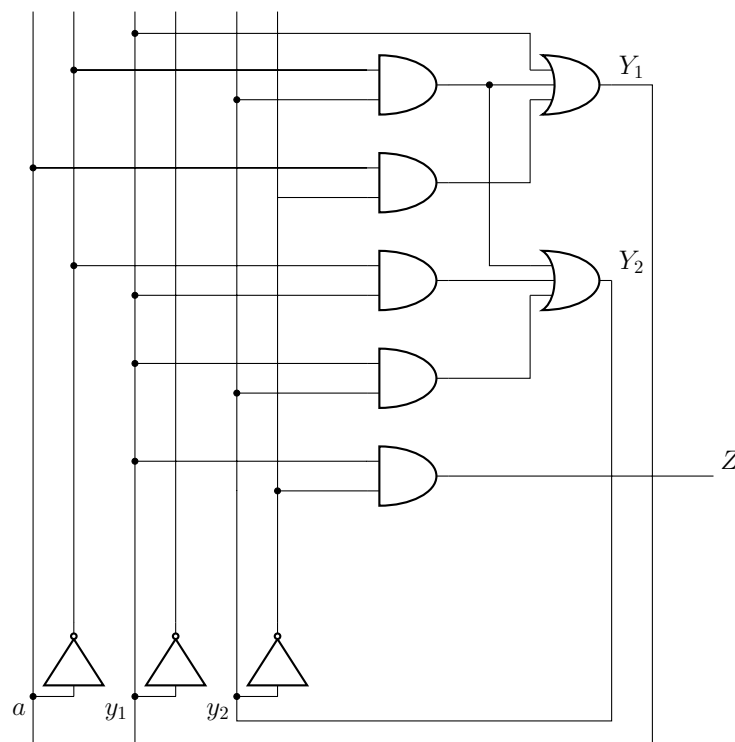


**Answer:**

$$Y_1 = y_1 + \bar{a}y_2 + a\bar{y}_2$$

$$Y_2 = \bar{a}y_2 + \bar{a}y_1 + y_1y_2$$

$$Z = y_1\bar{y}_2$$

	$a$		
$Y_1Y_2$	0	1	$Z$
00	00	10	0
01	11	00	0
11	11	11	0
10	11	10	1

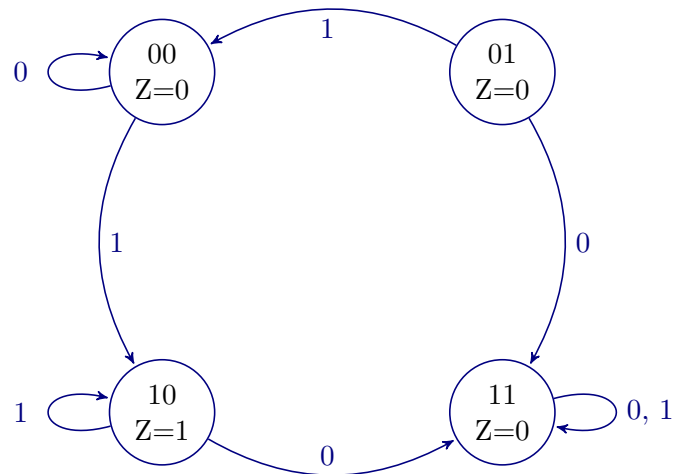

**Question 2.** A door opener is controlled by a password that is controlled using two buttons  $a$  and  $b$ . We assume that the value associated to each button equals 1 when the button is pressed, 0 otherwise. The door is being opened if the output  $Z_1$  is set to 1, which happens whenever the last button of the password is pressed. The code is the following: press and release  $a$  two times, then press and release  $b$  and finally press and release  $a$  again. Any wrong sequence sets the output  $Z_2$  to 1, triggering the alarm. Once activated, the alarm stays active whatever the input.


Build the state graph and Huffman table for this problem.


**Answer:**

	$ab$					
	00	01	11	10	$Z_1$	$Z_2$
1	<b>1</b>	9	9	2	0	0
2	3	9	9	<b>2</b>	0	0
3	<b>3</b>	9	9	4	0	0
4	5	9	9	<b>4</b>	0	0
5	<b>5</b>	6	9	9	0	0
6	7	<b>6</b>	9	9	0	0
7	<b>7</b>	9	9	8	0	0
8	1	9	9	<b>8</b>	1	0
9	<b>9</b>	<b>9</b>	<b>9</b>	<b>9</b>	0	1

	ab				Z1	Z2
	00	01	11	10		
1	1	9	9	2	0	0
2	3	9	9	2	0	0
3	3	9	9	4	0	0
4	5	9	9	4	0	0
5	5	6	9	9	0	0
6	7	6	9	9	0	0
7	7	9	9	2	0	0
8	1	9	9	8	1	0
9	9	9	9	9	0	1

↖ ↗  
état absorbant

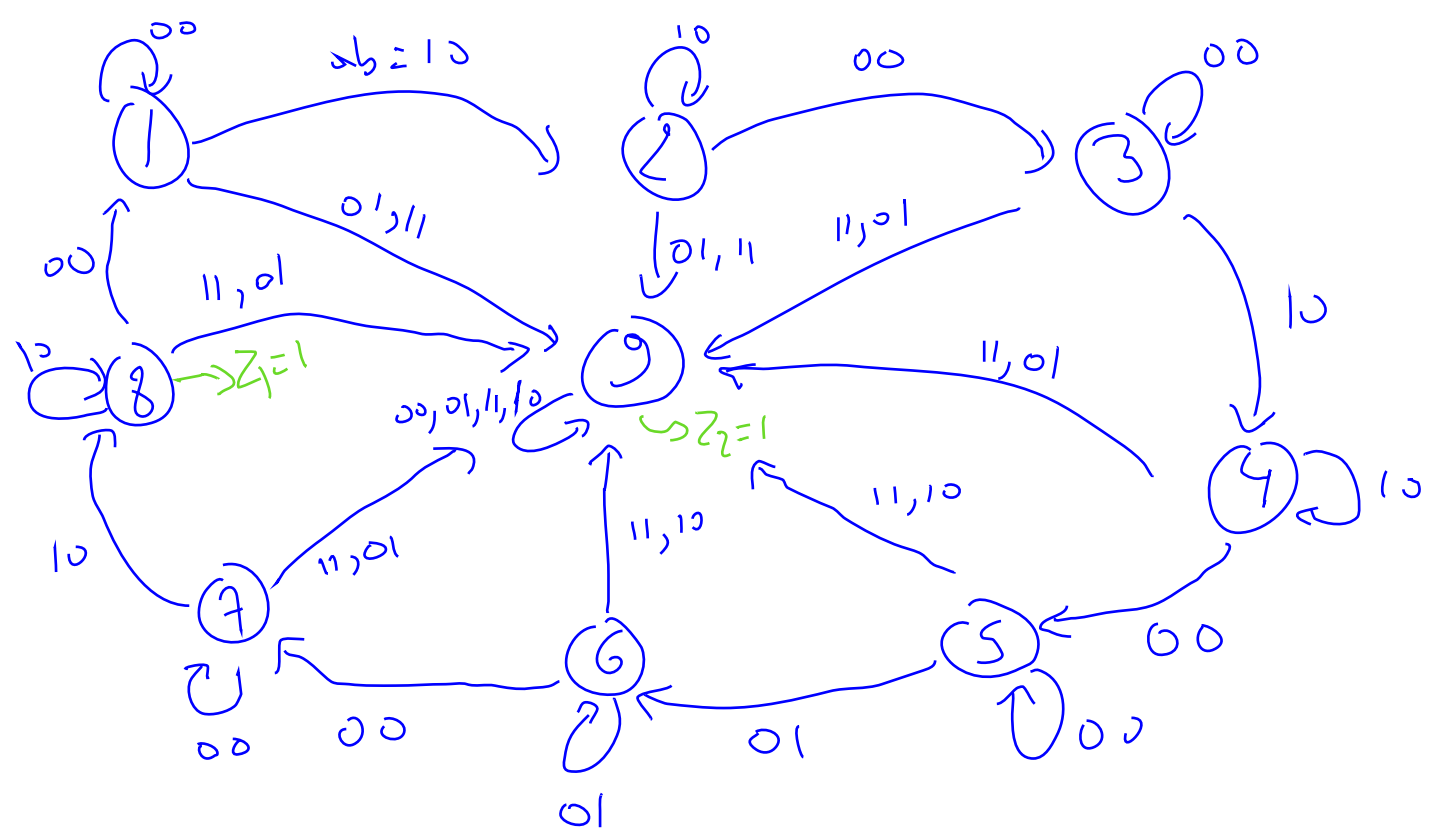

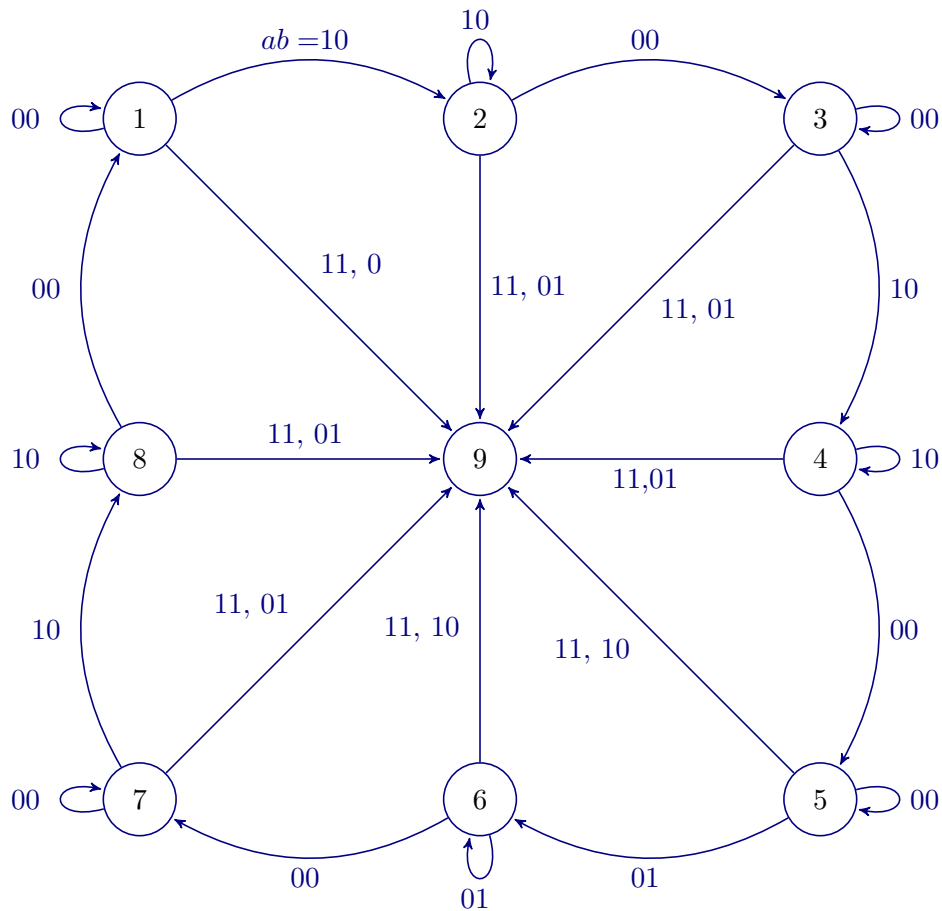

The state 9 is stable for all inputs. The retroaction loops have been omitted to keep the graph light, though

**Question 3.** Use a K-map to simplify the following equation:

$$f(a, b, c, d, e) = \sum_m (0, 2, 5, 7, 8, 9, 10, 11, 13, 23, 26, 27, 29) + \sum_d (3, 12, 15, 18, 19, 21, 22, 31)$$

**Answer:**

		abc								
de		000	001	011	010	100	101	111	110	
00		1	0	-	1	0	0	0	0	$F = \overline{a}c\overline{e} + ce + \overline{a}b\overline{c} + \overline{c}d$
01		0	1	1	1	0	-	1	0	
11		-	1	-	1	-	1	-	1	
10		1	0	0	1	-	-	0	1	

abc	000	001	011	010	100	101	111	110
00	1 0	0 4	- 12	1 8	0 16	0 20	0 28	0 24
01	0 1	1 5	1 13	1 9	0 17	- 21	1 29	0 25
11	- 3	1 7	- 15	1 11	- 19	1 23	- 31	1 27
10	1 2	0 6	0 14	1 10	- 18	- 22	0 30	1 26

=>

1	0	-	1	0	0	0	0
0	1	1	1	0	-	1	0
-	1	-	1	-	1	-	1
1	0	0	1	-	-	0	1